
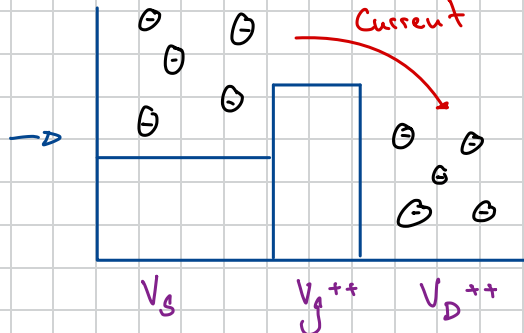
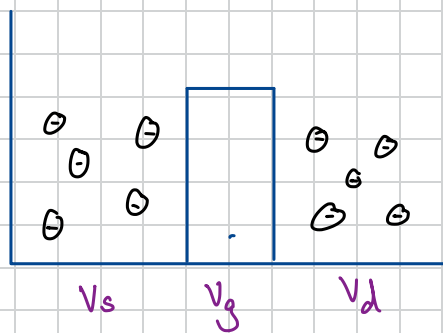


Lecture ①

→ Semiconductors & MOS-Transistors

Sidewiew of Silicon:

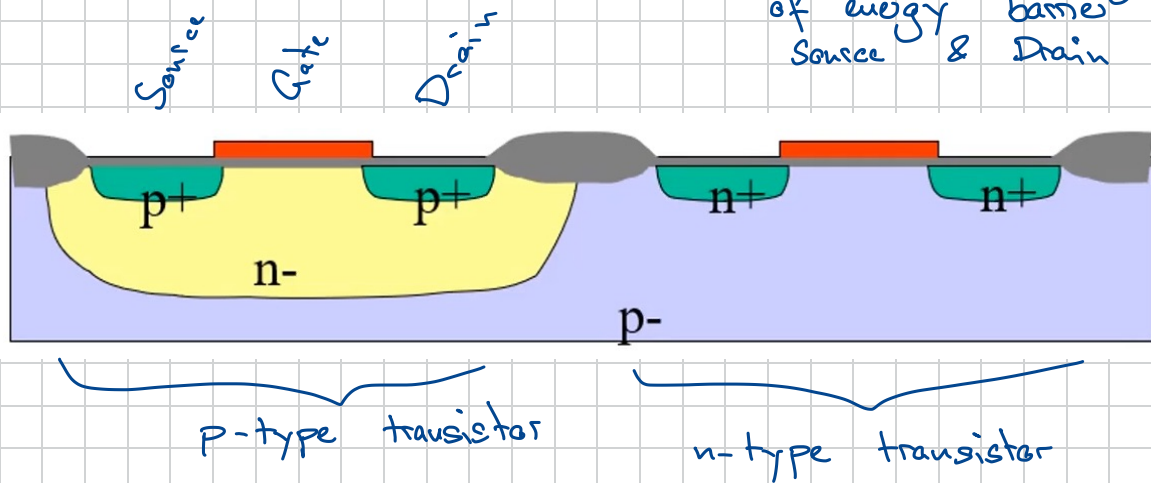→ Gate controls height of energy barrier between Source & Drain



→ Donors : Elements with $4 <$ electrons in outermost shell


→ Acceptors : Elements with $4 >$ electrons in outermost shell

→ Hole : Missing Electron → Quantum Mechanically behaves like a Particle

↳ Can move and so on like an electron

↳ Have positive Charge

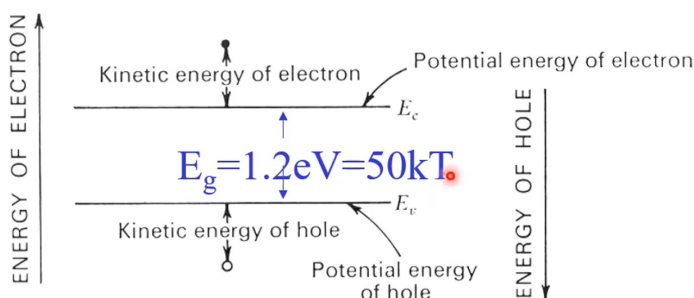↳ 2.5 times the effective charge of an electron



eV = electron Volts

k = Boltzmann Konstant


$$\hookrightarrow 1.38 \cdot 10^{-23} \frac{\text{J}}{\text{K}}$$

T = absolut Temperatur

The Fermi-Dirac Distribution

States above Fermi level are **occupied** with Boltzmann distribution

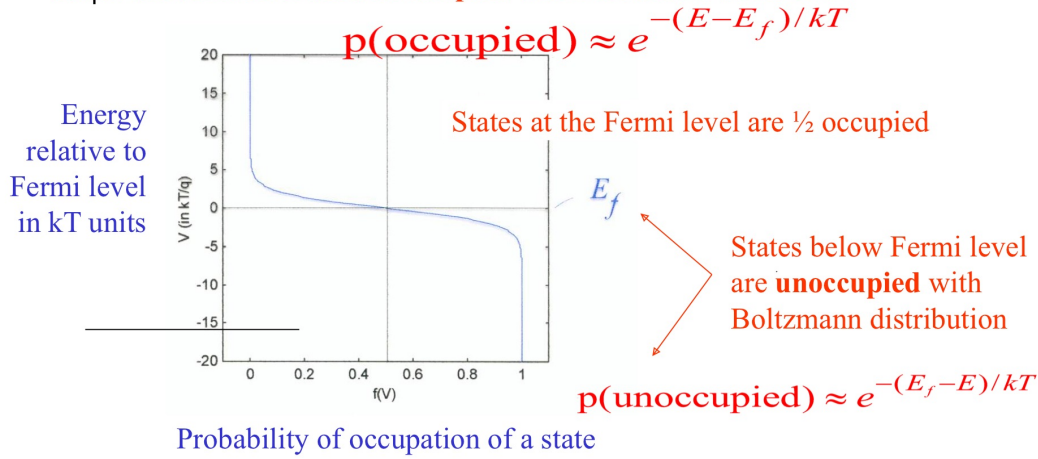→ describes distribution of Holes and electrons




→ Law of mass action: $n_p = n_i^2$

↳ the more holes, the less e^- and vice versa


Electron Movement:

① Drift:

eld

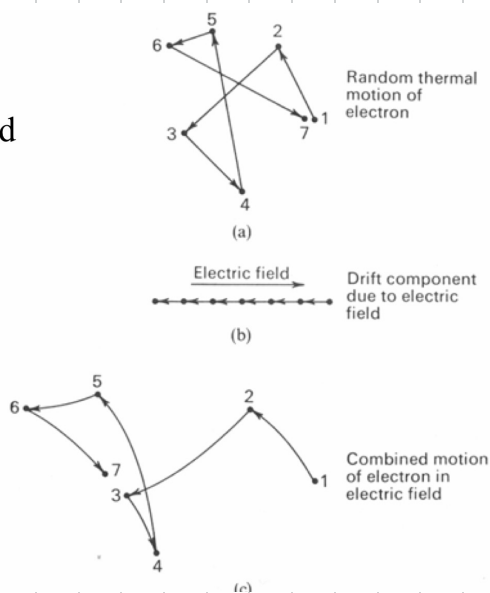

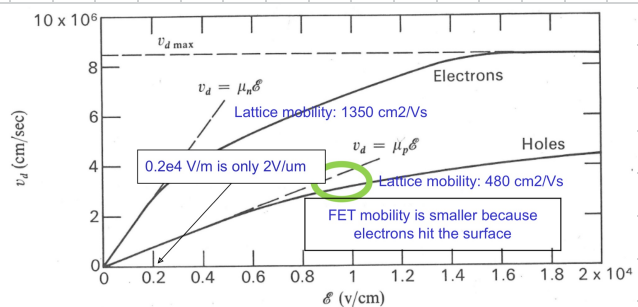→ Mobility is a function of the electric field



→ Random motion due to temp + electric field result in drift

Velocity

$$\vec{J} = qnv = qn\mu(\vec{\mathcal{E}})$$

□ Electric field

Current Flux

□

Mobility

□


Charge density

② Diffusion

→ function of concentration density

→ Drift & diffusion are related by Einstein Relation

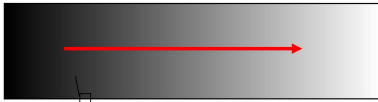Gray scale shows density of carriers that are moving at avg thermal velocity of ~100km/s



Diffusion current

$$\vec{J} = -Dq\nabla n$$

Current Flux

Diffusion constant

Spatial gradient of charge density

Drift and diffusion are related by the Einstein Relation

$$J_{\text{diffusion}} = -Dq\nabla n$$


$$J_{\text{drift}} = \mu q n \xi$$

→ n

$$D = \frac{kT}{q} \mu$$

D is proportional to absolute temperature T

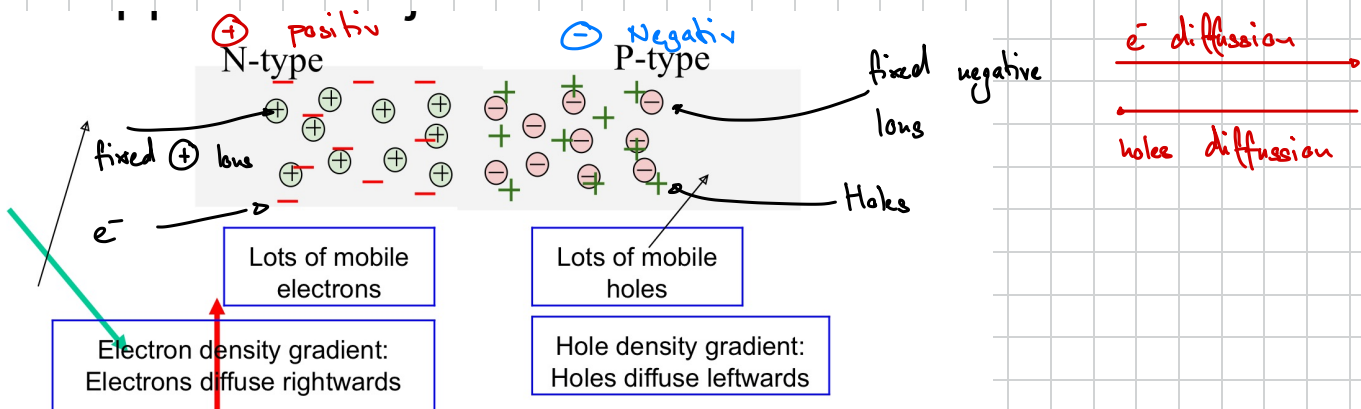Charges, fields, potentials in PN Junctions




The charge separation builds up an electric field to pull the carriers "back home"


In a PN junction with no applied voltage, drift and diffusion are balanced everywhere

Lecture 2


Symbols for transistors

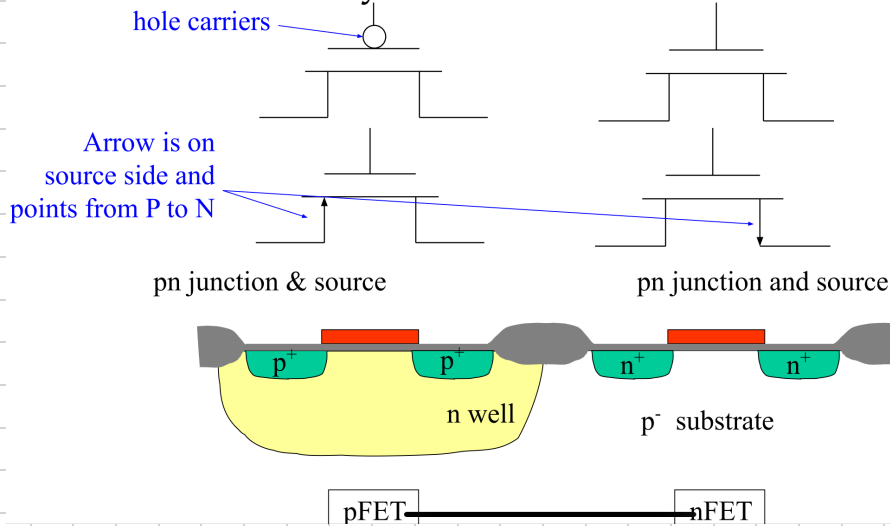


NMOS : $\rightarrow$ Carries e^-

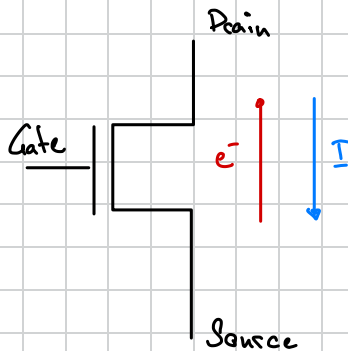

PMOS : $\rightarrow$ carries Holes

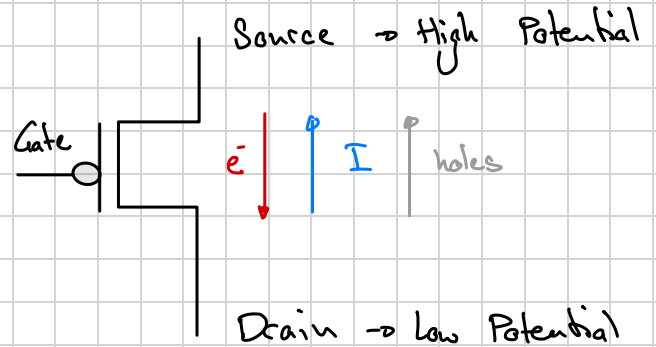

$\rightarrow$ Mistakes in Intro NB:

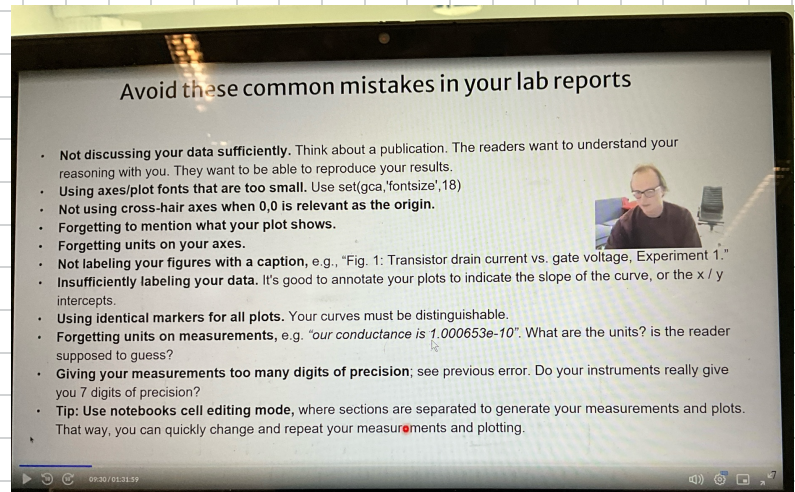

Constants :

q = charge of a electron


$V_T = kT/q \rightarrow$ Thermal voltage $\approx 26 \text{ mV}$

ϵ = Permittivity of vacuum



$$\text{Electric Field} = \frac{\sigma}{\epsilon_0 \epsilon_r}$$

σ $\rightarrow$ $\frac{Q}{A}$
 ϵ_0 $\rightarrow$ Permittivity of vacuum
 ϵ_r $\rightarrow$ relative permittivity



→ Fermi - Dirac Distribution:

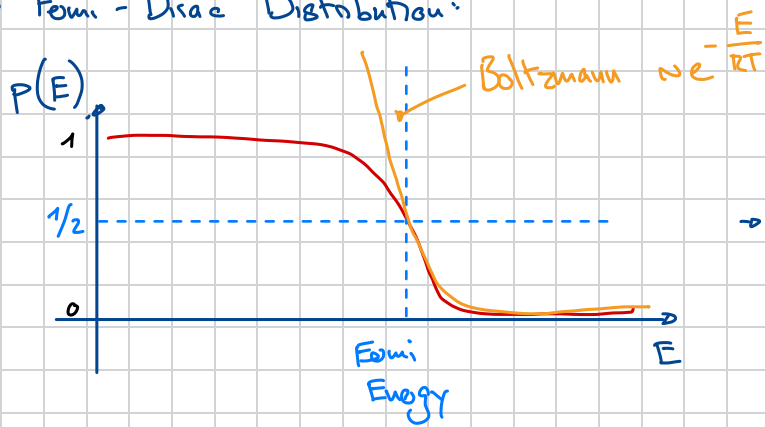

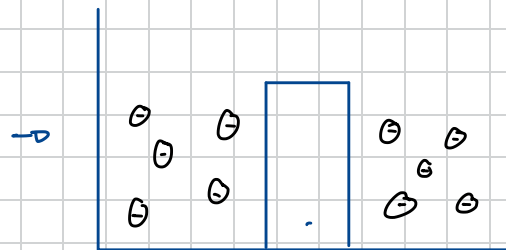
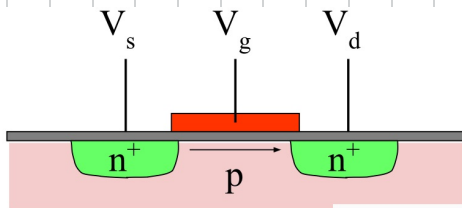
→ In areas of low Energy, it's very likely that an e^- appears



→ No Movement

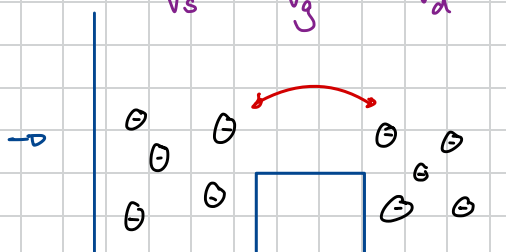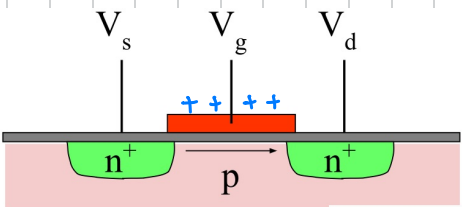

→ Movement but no net-Flow

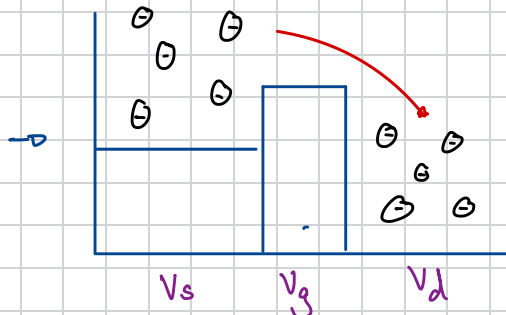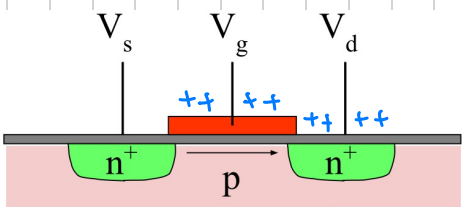

→ Net-flow from Source to drain

→ Low Energy
↳ higher probability that electrons are there

→ Similarity's between Neurons & Transistors

Neuron channels and Transistors



Both depend on exponential Boltzmann distributions of Concentration vs. Energy.

Neurons *needs much less voltage to activate*



- **Membrane ionic conductance** is exponentially dependent on the **voltage across the neuron membrane**.
- The **population of open channels** depends exponentially on potential across barrier.

Transistors

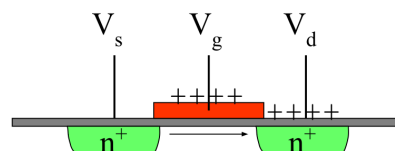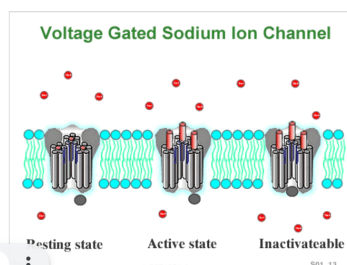
- **Current flow** in transistors is exponentially dependent on **barrier height**.
- The **population of carriers** depends exponentially on the barrier height.



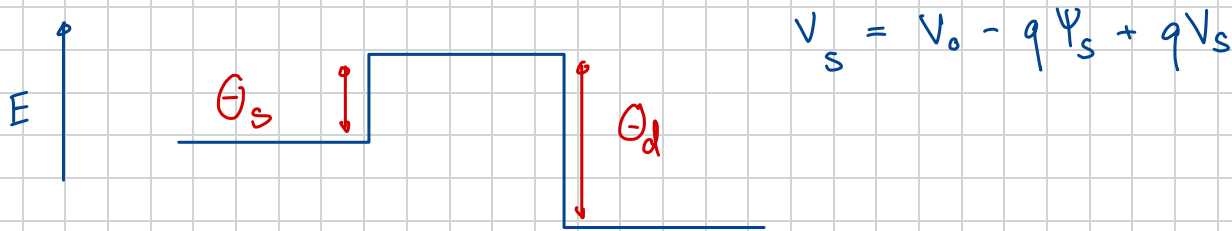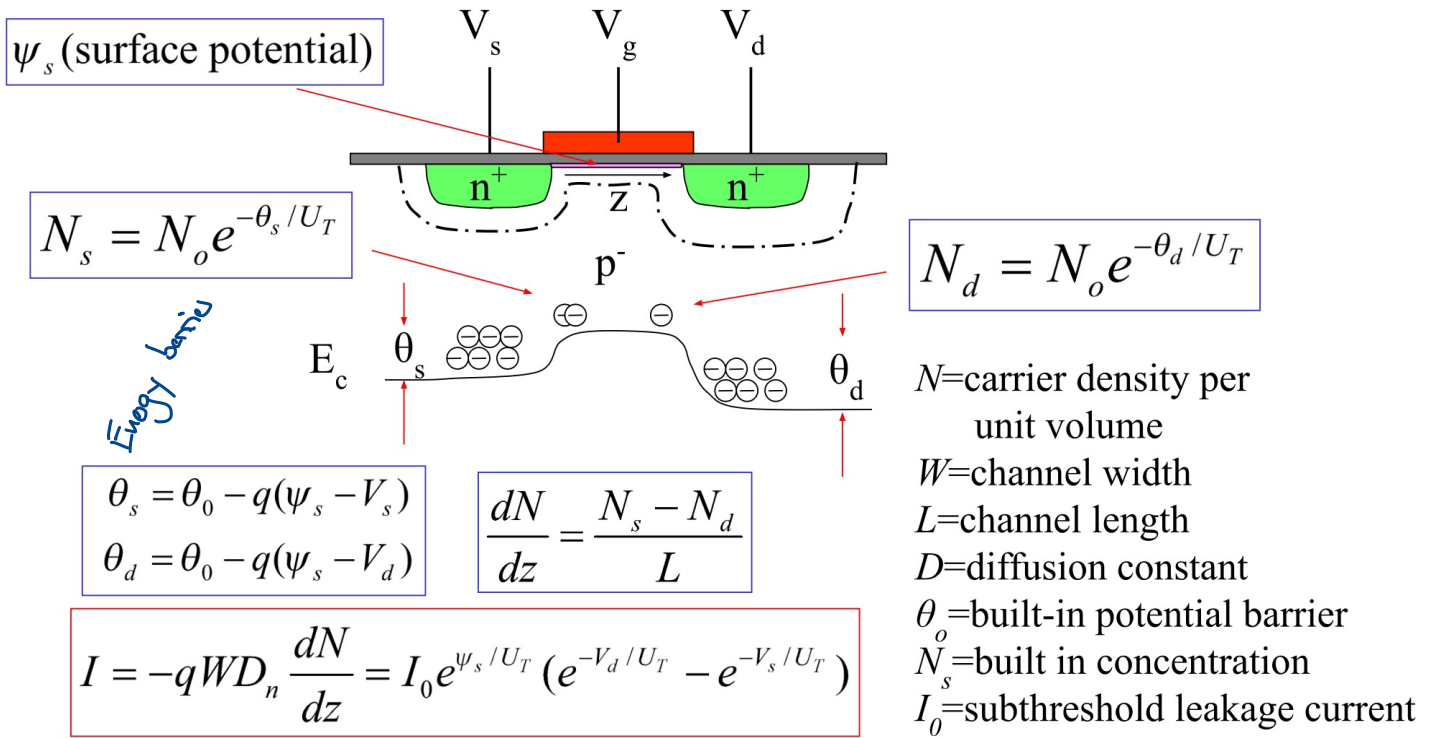Subthreshold nFET: Current is diffusion current



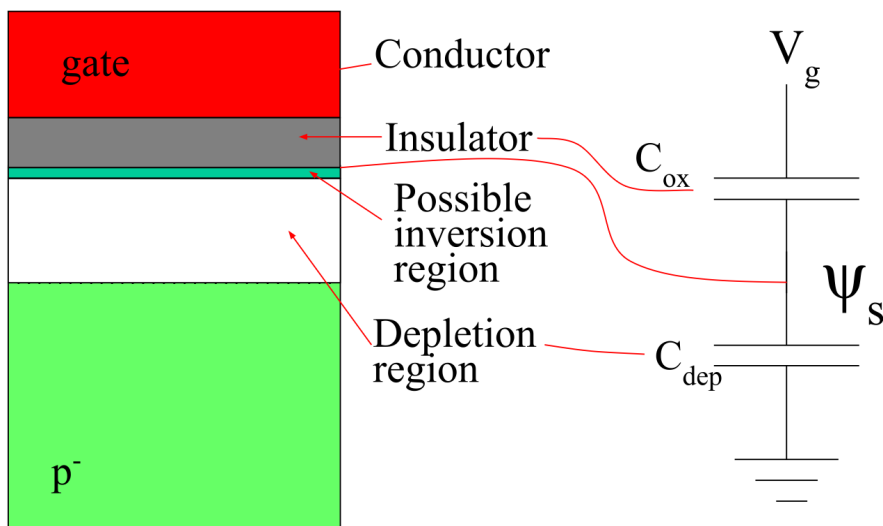Influence of gate on surface potential ψ_s





ψ_s is controlled only by V_g and the bulk voltage (ground for n-fet), through the capacitive divider C_{ox} and C_{dep}

$$\kappa(kappa) = \frac{\partial \psi_s}{\partial V_g} = \frac{C_{ox}}{C_{ox} + C_{dep}}$$

$\rightarrow \kappa = \frac{\text{rate change of Surface Potential}}{\text{Gate Voltage}}$

Puzzle Lecture ②:


→ Circuit calls "Source Follower"

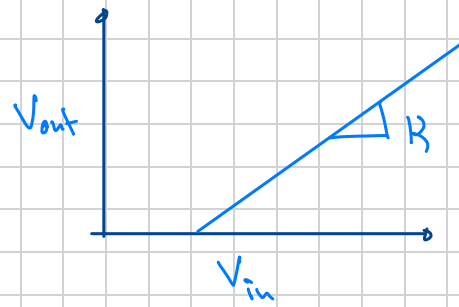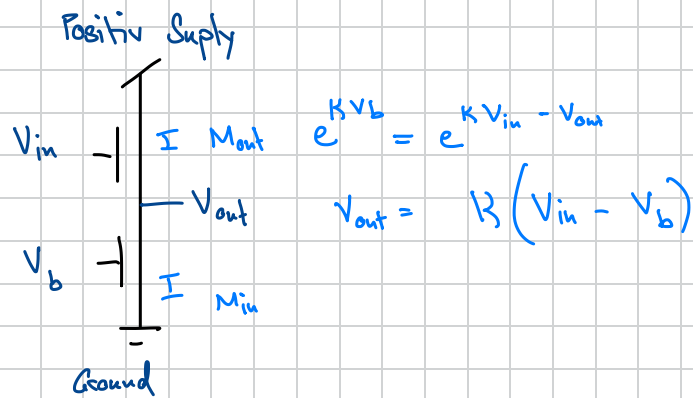



$$R = \frac{C_{ox}}{C_{ox} + C_{dep}}$$

Saturation bezieht sich auf V_{DS} -Value

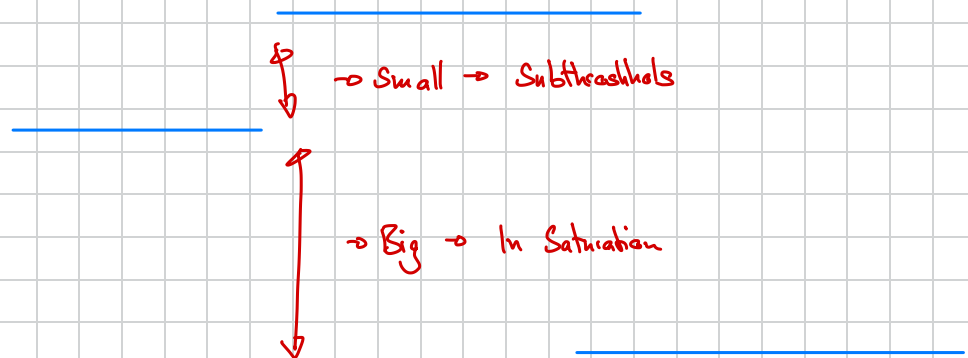Threshold bezieht sich auf: V_{GS} -Value




Lecture ③

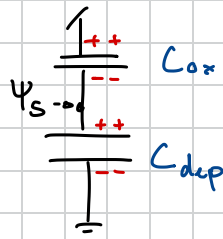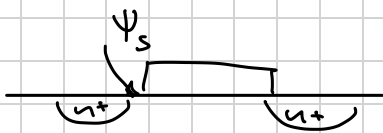

$$Q = C_{ox} (V_g - \psi_s) = C_{dep} \psi_s$$
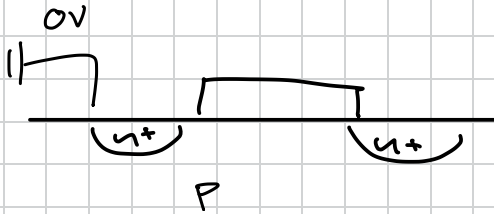
$$\psi_s = V_g \frac{C_{ox}}{C_{ox} + C_{dep}}$$



accumulation:

$$V_g < 0$$

Weak Inversion/depletion:

$$0 < V_g < V_T$$



Strong Inversion:

$$V_g > V_T$$


→ Small \$V_{ds}\$ $I_{ds} \text{ linear} = \mu E n = \mu \frac{V_{ds}}{L} (V_{gs} - V_T) C_{ox} W$

$$= \underbrace{\mu C_{ox} \frac{W}{L}}_{\beta} V_{ov} V_{ds}$$

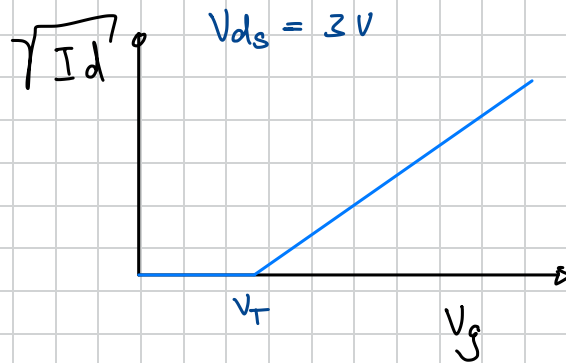
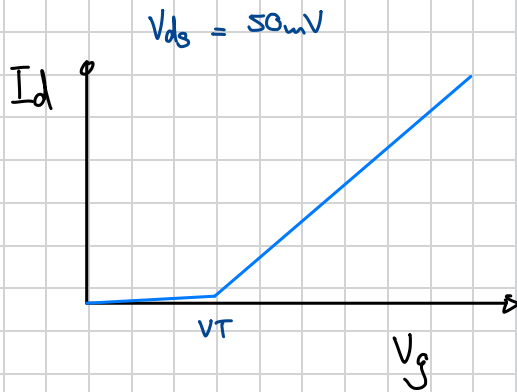
Overtime → how much \$V_{gs}\$ is over threshold
\$V_{ov}\$



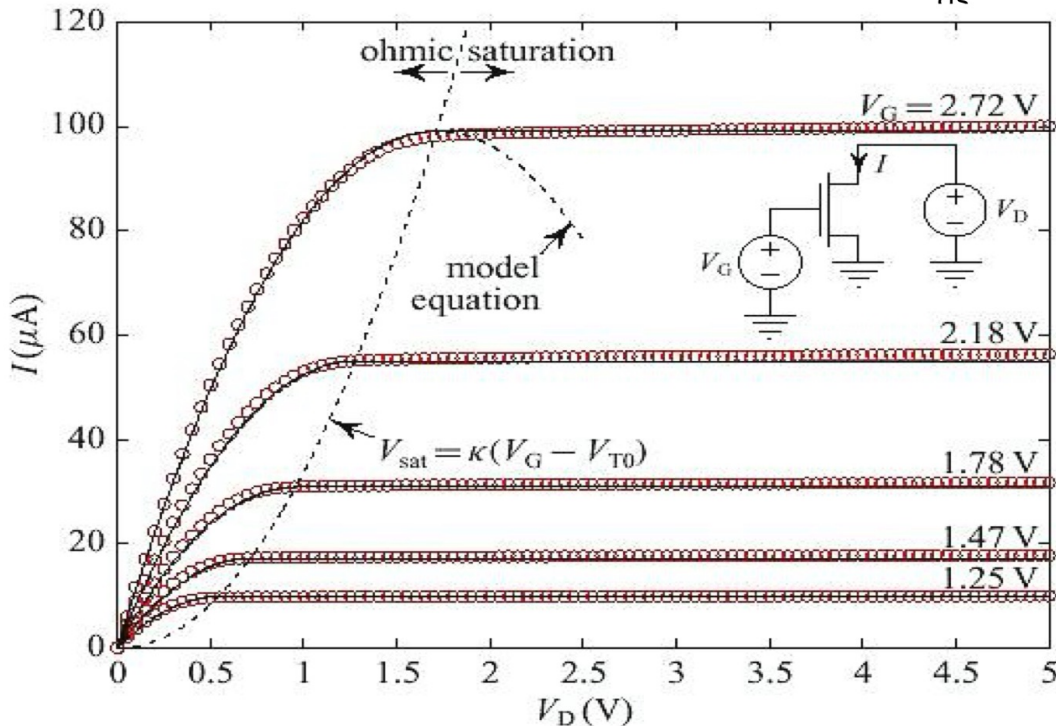Above Threshold nFET curve: \$I\$ vs \$V_{dc}\$



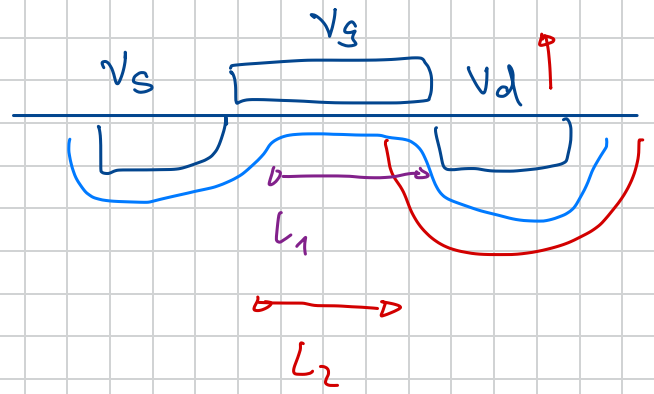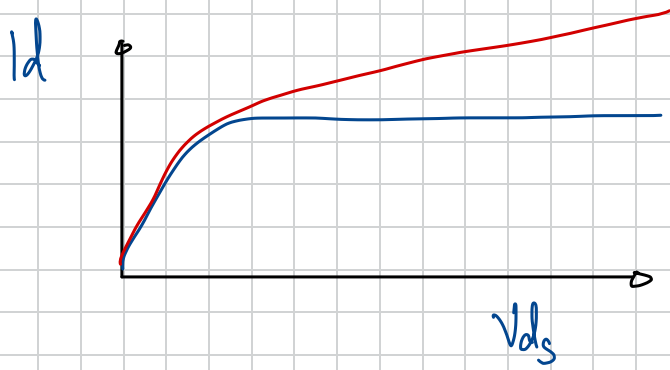→ the higher the gate voltage, the higher the current at saturation




→ Channel Length modulation
with rising V_d

→ "Early" effect


↳ Smaller "Shorter" Transistors are
more effected

Source Follower

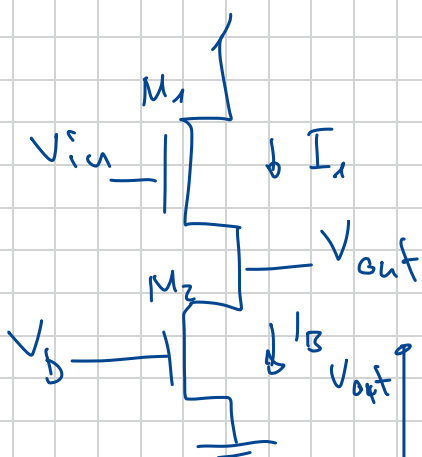


$$I_1 = I_B$$

$$V_{out} = k(V_{in} - V_{th})$$

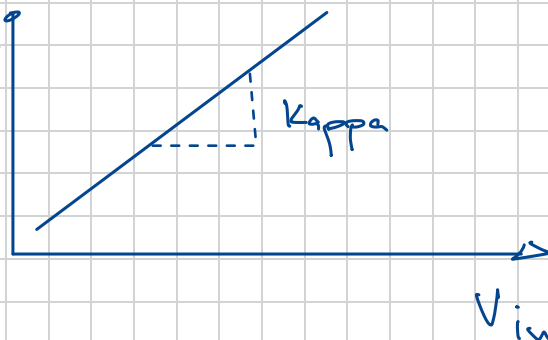

C2F:

$$f = \frac{I}{C \Delta v}$$

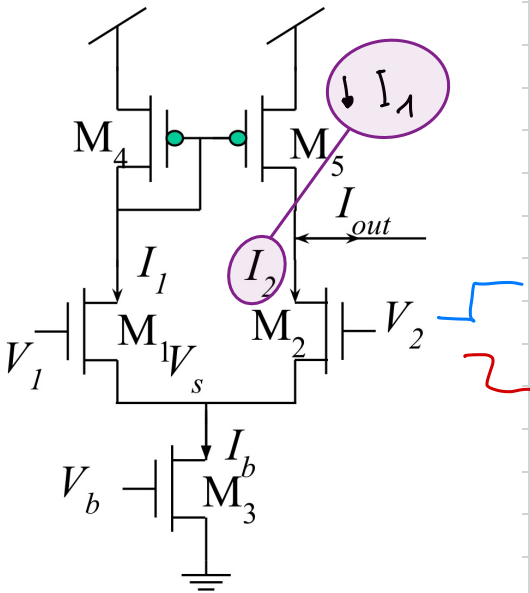

$$I_1 = \frac{I_b}{2} - \epsilon I$$


$$I_1 = \frac{I_b}{2} + \epsilon I$$

$$I_2 = \frac{I_b}{2} + \epsilon I$$

$$I_2 = \frac{I_b}{2} - \epsilon I$$

$\Rightarrow I_1 \neq I_2$ what means we have a change in the V_s of M_2


DVS Lab

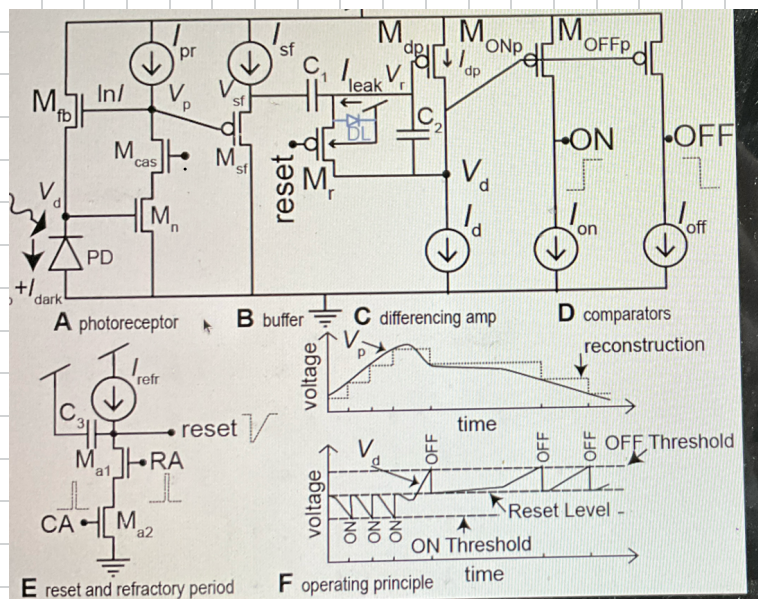


$$\begin{aligned} \Rightarrow C_1 V_{sf} &= \overbrace{\frac{-C_1 - C_2}{s}}^{\Rightarrow 0} V_d - C_2 V_d \\ V_d &= -\frac{C_1}{C_2} V_{sf} \end{aligned}$$

$$\rightarrow C_1 \left(V_{sf} + \frac{V_d}{A} \right) = C_2 \left(-\frac{V_d}{A} - V_d \right)$$

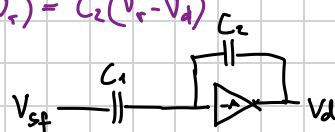Charge
→ $Q^* = C_1(V_{gs} - V_T) = C_2(V_T - V_d)$



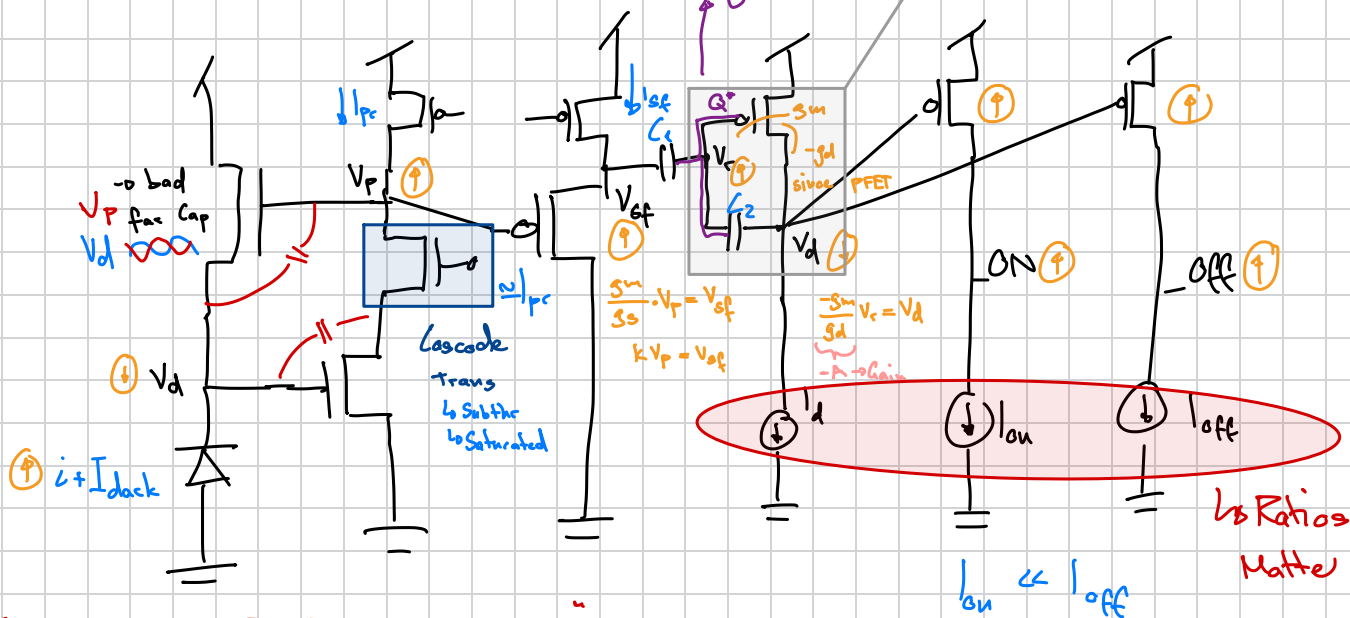In theory this charge is constant $\rightarrow$ Caps act as Memory




~~X~~ $\rightarrow$ Miller Caps: $\rightarrow$ Parasitic Capacitance


↳ Every trans is a bit of a Cap $\rightarrow$ Miller Capacitance is important since it is between two nodes that move apart

→ Cascode :

→ We have cap between two nodes that move apart

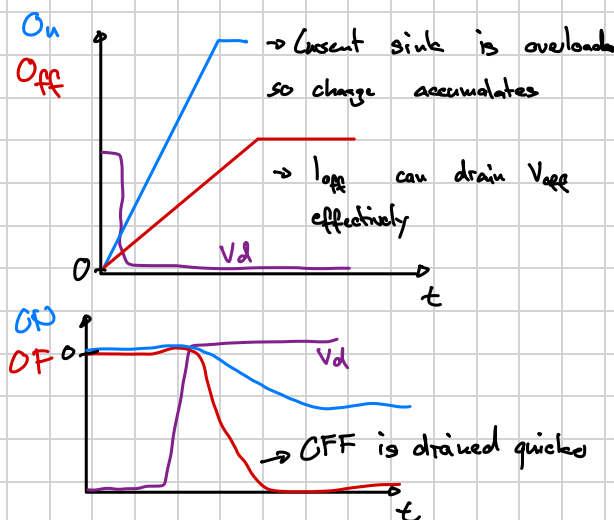
→ Cascode separates V_p of V_d by just putting a transistor in between



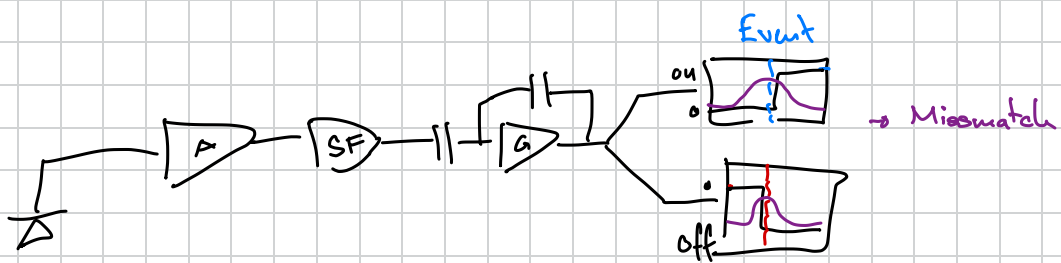

WTA

→ Current Correlators

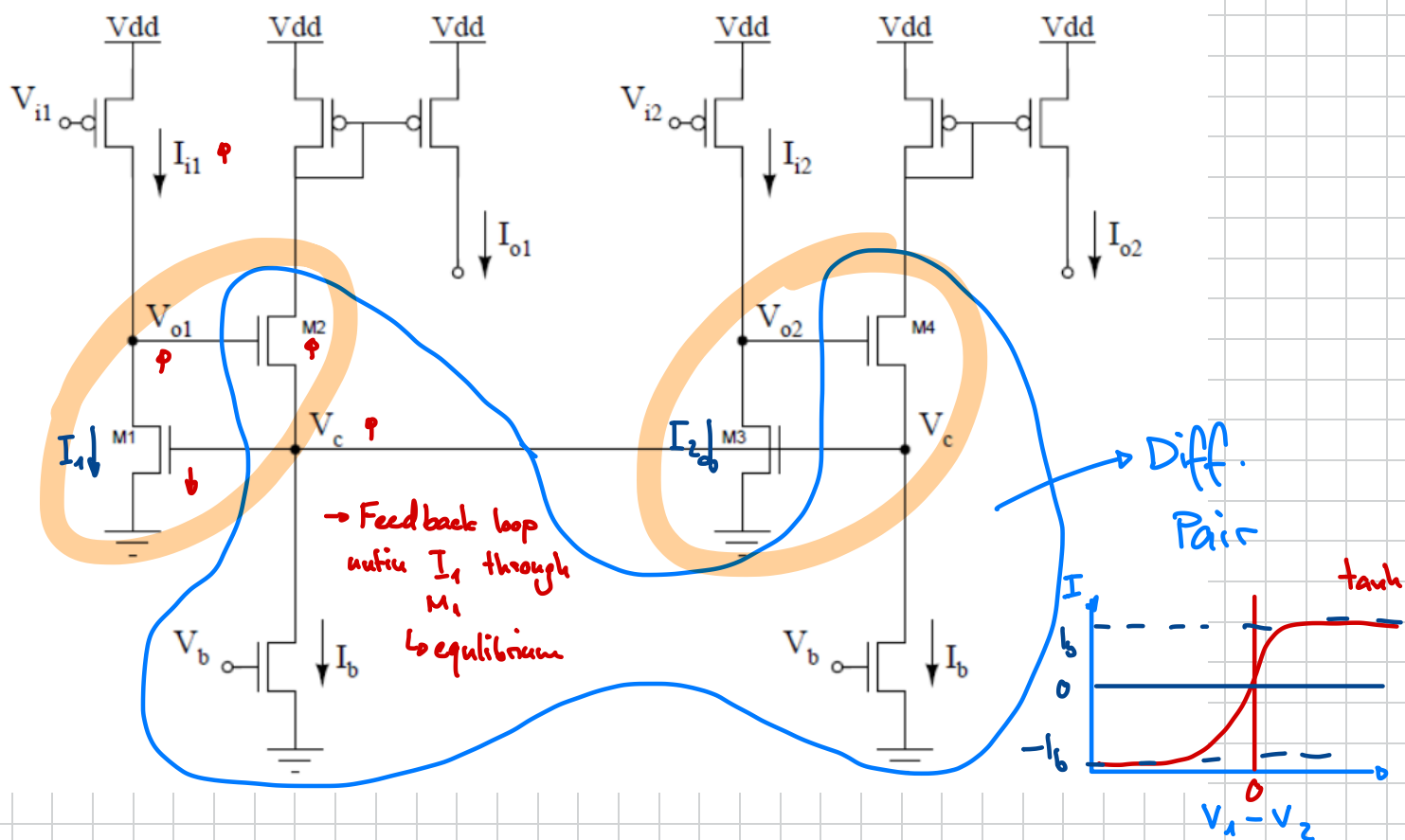


$$V_c \propto \ln\left(\frac{I_1}{I_0}\right) = \ln\left(\frac{I_2}{I_0}\right) \quad \text{if } I_1 = I_2$$

$$\rightarrow I_{o1} = I_{o2} = \frac{I_b}{2} \quad (\text{if } V_{o1} = V_{o2})$$

$$\hookrightarrow I_{oi} = \frac{I_b}{N}$$


↳ normally:
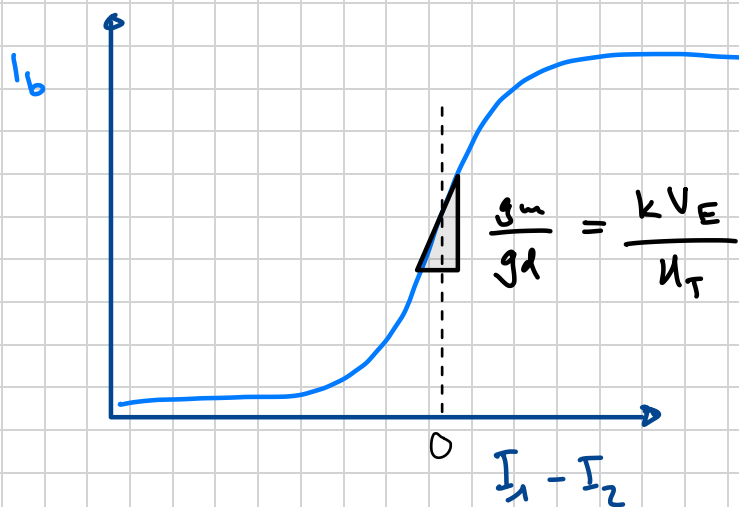
$$V_c = \max \ln\left(\frac{I_i}{I_0}\right)$$




→ Selectivity Gain
↳ speed of picking a winner

↳ determined by V_E

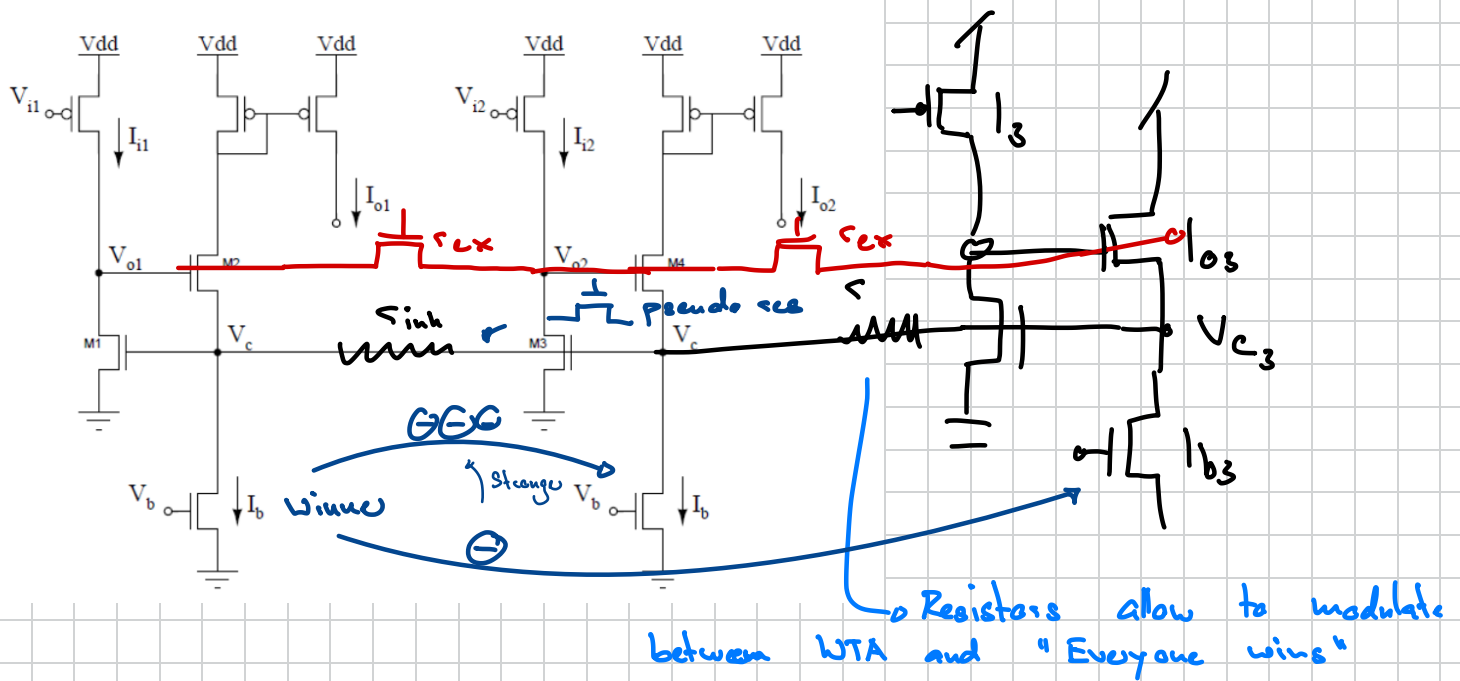

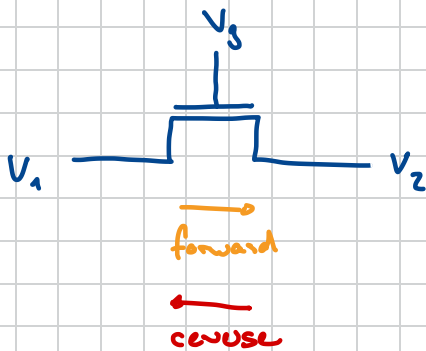→ Circuit influences more with less resistors in between
 ↳ Local contest → Local Inhibition



Subthreshold:

$$I_d = \underbrace{I_0 e^{kV_g - V_2}}_{\text{Forward}} - \underbrace{I_0 e^{kV_g - V_1}}_{\text{Reverse}}$$

↳ we want

$$I = G^* (V_1^* - V_2^*) \rightarrow \text{pseudo conductance}$$

$$I_d = \underbrace{I_0 e^{kV_g}}_{G^*} \left(\underbrace{e^{-V_2}}_{V_2^*} - \underbrace{e^{-V_1}}_{V_1^*} \right)$$

→ conductance


○ V_{o1}, V_{o2}, V_{o3} connected

↳ Everyone wins if $r=0$


↳ absolut WTA if $r=\infty$

↳ acts as excitatory center

→ Positive Feedback Loop

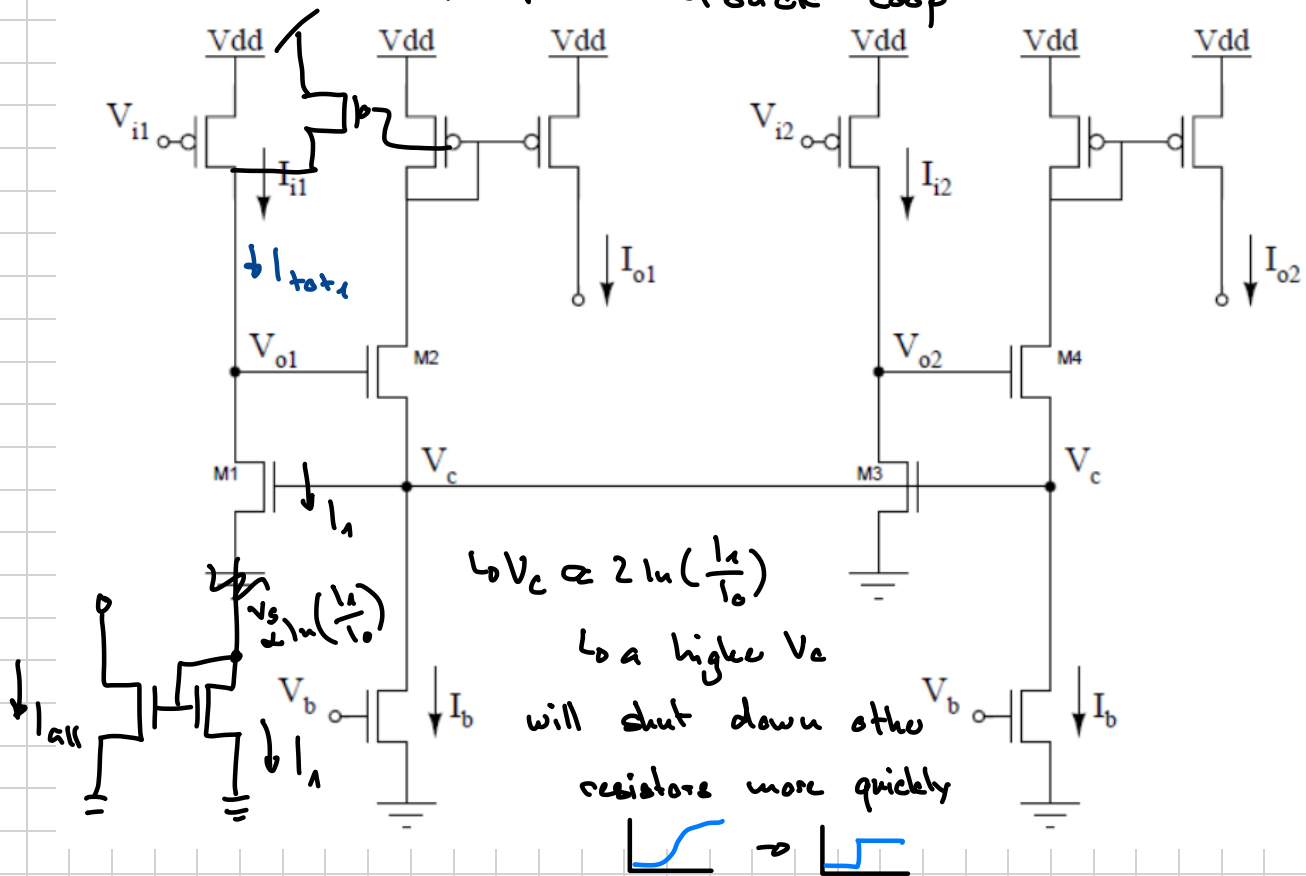

Hysteresis

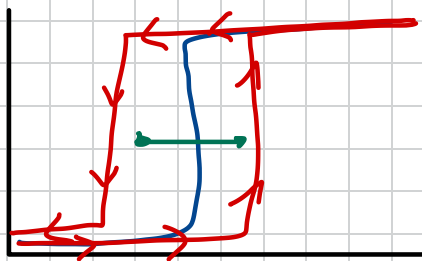

→ Winner can win more easily again

- State maintaining Machine

↳ Controllable over $\frac{W}{L}$ of PFET

Diode Source regeneration

→ To increase the selectivity of circuit




steep slope

→ increase in selectivity gain

Synapse

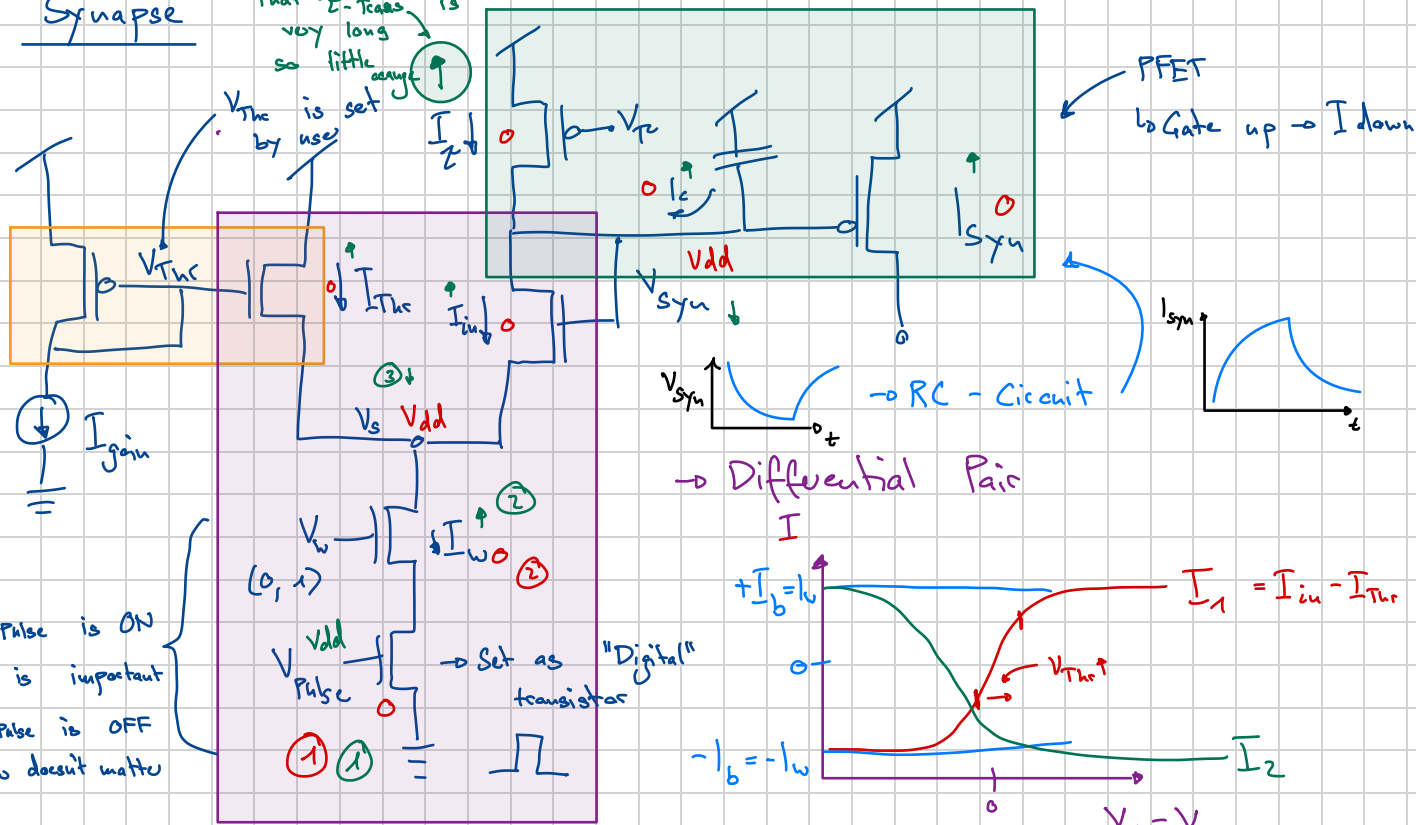We would assume that τ -Trans is very long so little change is



$\rightarrow$ Weird Current Mirror since PFET / NFET

$\hookrightarrow$ Inverse Relationship between I_{Th} & I_{gain}

A change in V_{Th} will affect I_{in}

When $V_{pulse} = V_{dd}$:

$$\rightarrow I_{Th} + I_{in} = I_w$$

$$\rightarrow I_w = \underbrace{I_0 e^{k V_{Th} - V_s}}_{I_{Th}} + \underbrace{I_0 e^{k V_{syn} - V_s}}_{I_{in}}$$

$$\rightarrow I_{in} = I_c + I_c$$

$$\rightarrow I_0 e^{k V_{syn} - V_s} = I_c + I_c$$

$$(1) \quad I_0 e^{-V_s} = \frac{I_w}{e^{k V_{Th}} + e^{k V_{syn}}}$$

$$(2) \quad \rightarrow I_w \frac{e^{k V_{syn}}}{e^{k V_{syn}} + e^{k V_{Th}}} = I_c + I_c$$

$$(3) \quad \rightarrow I_c = \left(\frac{\partial (V_{dd} - V_{syn})}{\partial t} \right) = - \left(\frac{\partial V_{syn}}{\partial t} \right)$$

chain Rule

$$\rightarrow I_{syn} = I_0 e^{-k V_{syn} + V_{dd}}$$

$$\rightarrow \frac{\partial I_{syn}}{\partial t} = \frac{\partial I_{syn}}{\partial V_{syn}} \frac{\partial V_{syn}}{\partial t}$$

$$\frac{\partial I_{syn}}{\partial t} = -k I_{syn} \frac{\partial V_{syn}}{\partial t}$$

$$\rightarrow I_w \frac{1}{1 + e^{k V_{Th}} \cdot e^{-k V_{syn}}} = I_c + I_c$$

divide by $e^{k V_{syn}}$

$$\rightarrow I_w \frac{1}{1 + \frac{e^{-k V_{Th}}}{e^{k V_{syn}}}} = I_c + I_c$$

$$(4) \quad - \frac{\partial V_{syn}}{\partial t} = \frac{1}{k I_{syn}} \frac{\partial I_{syn}}{\partial t}$$

$$\rightarrow I_w \frac{1}{1 + \frac{I_{syn}}{I_0 e^{-k_e V_{thr}} + V_{dd}}}$$

$$\textcircled{5} \rightarrow I_w \frac{1}{1 + \frac{I_{syn}}{I_{gain}}}$$

$$\textcircled{6} \quad I_w \frac{1}{1 + \frac{I_{syn}}{I_{gain}}} = I_r + \frac{C}{k I_{syn}} \frac{\partial I_{syn}}{\partial t}$$

divide by I_r
multiply by I_{syn}

$$\rightarrow \frac{I_w}{I_r} \frac{I_{syn}}{1 + \frac{I_{syn}}{I_{gain}}} = I_{syn} + \frac{C}{k I_r} \frac{\partial I_{syn}}{\partial t}$$

can be ignored

if $I_w \gg I_r$

$$\rightarrow \frac{I_w I_{gain}}{I_r} = I_{syn} + \tau \frac{\partial I_{syn}}{\partial t}$$

$\hookrightarrow$ Lowpass Filter